

# HW4\_EE\_5601\_code

October 21, 2024

```
[9]: import numpy as np
import math
pi = math.pi

#Prints out numbers without "np.flat64" displaying
np.set_printoptions(legacy='1.25')
```

## 0.1 Problem 4.14

a) is network lossless?

```
[10]: def pol2comp(mag,ang) :
    a = mag*math.cos(math.radians(ang))
    b = mag*math.sin(math.radians(ang))
    if a < 10**-15 :
        a = 0
    if b < 10**-15 :
        b = 0
    output = complex(a,b)
    return output

S11 = pol2comp(0.178,90)

S = np.matrix([[pol2comp(0.178,90),pol2comp(0.6,45),pol2comp(0.
↵4,45),0],[pol2comp(0.6,45),0,0,pol2comp(0.3,-45)],[pol2comp(0.
↵4,45),0,0,pol2comp(0.5,-45)],[0,pol2comp(0.3,-45),pol2comp(0.5,-45),0]])
S_conj = S.conjugate()
S_squared = np.matmul(S,S_conj)

print_matrix = S
print('S = ')

for i in range(0,len(print_matrix)) :
    string = '|'
    for j in range(0,len(print_matrix)) :
        val = 'S' + str(i+1) + str(j+1)
        string = string + val
    if j != len(print_matrix)-1 : string = string + ','
```

```

        if len(val) < 15 :
            l = len(val)
            while l<15 :
                string = string + ' '
                l+=1
            if j == len(print_matrix)-1 : string = string + '||'
        print(string)

print(' = ')

for i in range(0,len(print_matrix)) :
    string = '||'
    for j in range(0,len(print_matrix)) :
        val = str(np.round(print_matrix[i,j],3))
        string = string + val
        if j != len(print_matrix)-1 : string = string + ','
        if len(val) < 15 :
            l = len(val)
            while l<15 :
                string = string + ' '
                l+=1
        if j == len(print_matrix)-1 : string = string + '||'
    print(string)

```

```

S =
|S11,          S12,          S13,          S14          |
|S21,          S22,          S23,          S24          |
|S31,          S32,          S33,          S34          |
|S41,          S42,          S43,          S44          |
=
|0.178j,       (0.424+0.424j), (0.283+0.283j), 0j      |
|(0.424+0.424j), 0j,          0j,          (0.212+0j)   |
|(0.283+0.283j), 0j,          0j,          (0.354+0j)   |
|0j,           (0.212+0j),     (0.354+0j),    0j      |

```

S is not idntiy matrix, therefore this network is not lossless.

b) Network is reciprocal.

c) Return Loss?

```

[11]: S11 = 0.178
      RL = -20*math.log10(S11)
      print(f'c) Return Loss = {RL}')

```

c) Return Loss = 14.99159995382212

d) Insertion Loss and

```
[12]: S42 = 0.3
      IL = -20*math.log10(S42)
      print(f'Insertion Loss = {np.round(IL,2)} dB')
      print('Phase Delay = 45 degrees')
```

Insertion Loss = 10.46 dB

Phase Delay = 45 degrees

- e) Reflection coefficient @P1, with short @P3, and all other ports terminated with matched loads.

```
[13]: S11 = S[0,0]
      S13 = S[0,2]
      S31 = S[2,0]

      Ref = S11 - S13*S31
      print(f'Reflection Coefficient = {np.round(Ref,3)}')
```

Reflection Coefficient = 0.018j

## 0.2 Problem 4.20

```
[25]: ZL = 100
      Zo = 70.7
      Zg = 100
      Vo = 30
      B1 = math.radians(90)

      Zin = np.round(Zo*(complex(ZL,(Zo*math.tan(B1))))/(complex(Zo,(ZL*math.
      ↪tan(B1)))),1)

      a = Vo*np.sqrt(Zin)/(Zin+Zg)
      PL = 0.5*(abs(a)**2)
      print(f'a = {np.round(a,3)}')
      print(f'PL = {np.round(PL,3)}')
```

a = (1.414+0j)

PL = 1.0

## 0.3 Problem 4.24

```
[17]: #Source Parameters
      R = 50

      A1 = 1
      B1 = R
      C1 = 0
      D1 = 1
      ABCD1 = np.matrix([[A1, B1],[C1,D1]])
```

```

print('Source Resistor ABCD parameters')
print(f'{A1} {B1}')
print(f'{C1} {D1}')
print('')

#Transformer Parameters
N = 1/2

A2 = N
B2 = 0
C2 = 0
D2 = 1/N
ABCD2 = np.matrix([[A2,B2],[C2,D2]])

print('Transformer ABCD parameters')
print(f'{A2} {B2}')
print(f'{C2} {D2}')
print('')

#Tline parameters
Zo3 = 50 #ohms
B13 = 90 #degrees

Yo3 = 1/Zo3
A3 = complex(round(math.cos(math.radians(B13)),4),0)
B3 = complex(0,round(Zo3*math.sin(math.radians(B13)),4))
C3 = complex(0,round(Yo3*math.sin(math.radians(B13)),4))
D3 = complex(round(math.cos(math.radians(B13)),4),0)
ABCD3 = np.matrix([[A3, B3],[C3,D3]])

print('T-line ABCD parameters')
print(f'{A3} {B3}')
print(f'{C3} {D3}')
print('')

#Load Resistor
R_L = 25

A4 = 1
B4 = 0
C4 = 1/R_L
D4 = 1
ABCD4 = np.matrix([[A4,B4],[C4,D4]])

```

```

print('Load ABCD parameters')
print(f'{A4} {B4}')
print(f'{C4} {D4}')
print('')

#Multiply all ABCD matrices together in order.
ABCD = np.matmul(ABCD1,ABCD2)
ABCD = np.matmul(ABCD,ABCD3)
ABCD = np.matmul(ABCD,ABCD4)

print('Final System Parameters')
print(ABCD)

```

Source Resistor ABCD parameters

```

1 50
0 1

```

Transformer ABCD parameters

```

0.5 0
0 2.0

```

T-line ABCD parameters

```

0j 50j
0.02j 0j

```

Load ABCD parameters

```

1 0
0.04 1

```

Final System Parameters

```

[[0. +3.j   0.+25.j ]
 [0. +0.04j 0. +0.j  ]]

```